
EMMAN ACE G. MENION BSCPE 3A


BCD DOWN COUNTER:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
entity practice is
Port (
                            -- Clock (PIN_23)
  clk : in STD_LOGIC;
  reset n:in STD LOGIC;
                                   -- Active-low reset (PIN 25)
  bcd out: out STD LOGIC VECTOR(3 downto 0) -- QD,QC,QB,QA (MSB to LSB)
);
end practice;
architecture Behavioral of practice is
  signal counter : unsigned(3 downto 0) := "1001"; -- Start at 9
  signal slow_clk : STD_LOGIC := '0';
  signal clk divider: unsigned(24 downto 0) := (others => '0'); -- For 2Hz @ 50MHz
begin
  -- Clock divider for visible counting (2Hz)
  process(clk)
  begin
    if rising_edge(clk) then
      if clk divider = 12499999 then
        clk_divider <= (others => '0');
        slow_clk <= not slow_clk;
        clk divider <= clk divider + 1;
      end if;
    end if;
  end process;
  -- BCD Down Counter Logic
  process(reset_n, slow_clk)
  begin
    if reset_n = '0' then
      counter <= "1001"; -- Reset to 9
    elsif rising_edge(slow_clk) then
      if counter = "0000" then
        counter <= "1001"; -- Reset to 9
      else
        counter <= counter - 1;</pre>
      end if;
    end if;
  end process;
```

-- Active-low LED output (0=LED ON, 1=LED OFF)
bcd_out <= not std_logic_vector(counter);</pre>

end Behavioral;

 

 

Clock	QD	QC	QB	QA
0	1	0	0	1
1	1	0	0	0
2	0	1	1	1
3	0	1	1	0
4	0	1	0	1
5	0	1	0	0
6	0	0	1	1
7	0	0	1	0
8	0	0	0	1
9	0	0	0	0