

EMMAN ACE G. MENION

BSCPE 3A

VHDL CODE FOR JK FLIP FLOP WITH ASYNCHRONOUS RESET:

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity Binary_Gray is

port (

b : in std_logic_vector(3 downto 0); -- Binary input

g : out std_logic_vector(3 downto 0) -- Gray code output

);

end Binary_Gray;

architecture Behavioral of Binary_Gray is

begin

-- Gray code calculation:

-- MSB is same, others are XOR of adjacent bits in binary input


 
 

g(3) <= b(3);

g(2) <= b(3) xor b(2);

g(1) <= b(2) xor b(1);

g(0) <= b(1) xor b(0);

end Behavioral;

Reset	J	K	Clock	Q _{n+1}	$\overline{Q_n + 1}$	Status
1	X	X	X	0	1	Reset
0	0	0		Q _n	$\overline{Q_n}$	No Change
0	0	1		0	1	Reset
0	1	0		1	0	Set
0	1	1		$\overline{Q_n}$	Q _n	Toggle

